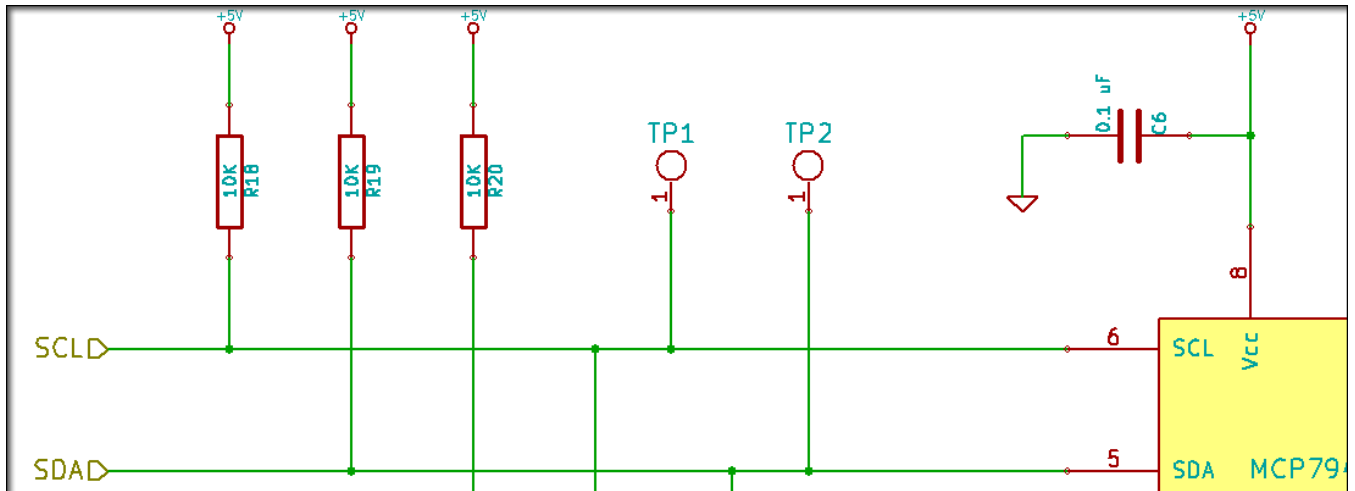


## I2C Pull Up Resistors



(<https://rheingoldheavy.com/wp-content/uploads/2015/01/Featured-29.png>)

In the previous module, we covered the I2C Basics. Now we're going to look at the pull up resistors in greater detail to understand their function and how they can be precisely sized.

### Objectives

1. Understand what is meant by a pull up resistor.
2. Understand what pull up resistors do in an I2C circuit.
3. Be able to calculate the lowest  $R_P$  using  $V_{OL}$  and  $I_{OL}$ .
4. Understand the concept of bus rise time.
5. Understand what is meant by bus capacitance and how pull up resistors interact with it.
6. Be able to calculate the highest  $R_P$  using all the elements of  $C_{BUS}$ .

### Background

I2C Basics (<http://rheingoldheavy.com/i2c-basics/>)

Reading through the previous sections will be helpful for the less experienced, but are not necessarily essential.

### Schematic

No schematic is associated with this module.

### Setup

This module is dedicated to I2C theory, so no hardware is necessary at this point.


## I2C Pull Up Resistors

As discussed in the I2C Basics module, the resistors that are commonly seen on I2C circuits sitting between the SCL and SDA lines and the voltage source are called pull up resistors. But what is a pull up resistor?

A pull up resistor is used to provide a default state for a signal line or general purpose input/output (GPIO) pin. Typically they are of high resistance thousands or tens of thousands of ohms of resistance. The high resistance ensures that you're not vampirically sucking too terribly much current on a constant basis through your resistor into your system ( $5V V_{dd} / 10000\Omega = 0.5mA$  current), and in fact the Arduino's main chip, the Atmel ATMEGA328P

has internal 20K pull up resistors that can be enabled through code to preset the GPIO pins to a logic high state.

In the case of I2C, the circuitry internal to the SCL and SDA processing subsystems of the chips you'll use are "open drain", which means they can sink current, but have no way of sourcing current. That means you supply it to them in the form of the logic high voltage of your circuit, which in the case of the Arduino Uno is typically 5V. In order to establish this high voltage, you attach a pull up resistor between 5V and the SCL and the SDA buses respectively. This is the graphic from the previous module describing that...

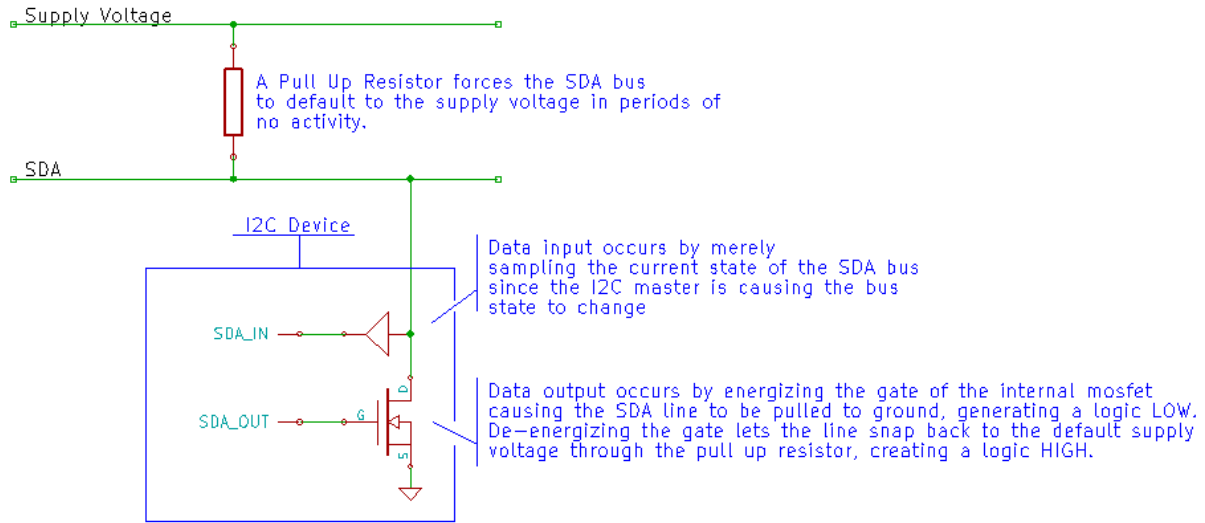

I2C PULL UP RESISTOR EXPLANATION

However, you can't just start whacking giant resistors in. There are several things that those resistors interact with that will help to determine what size of a pull up resistor you'll need.

### I2C Logical High and Low

The "Low Input Level Voltage",  $r_L$ , is  $0.3 \times V_{DD}$   
 the "High Input Level Voltage",  $r_H$ , is  $0.7 \times V_{DD}$

So, when we hook everything up to our Arduino, we need to ensure that our SCL and SDA lines are above 3.5V to register as a logic high signal, and below 1.5V to register as a logic low signal. Everything in between is... well... **HIC SVNT DRACONES.**

However, you have to achieve a certain amount of voltage, in order to even get the internal mosfet to conduct on your I2C bus, but not so much that we burn out the pin. Think of it like the LED voltage drop. If you have a 1.7V drop across your LED, it won't light up unless you supply some voltage greater than that, but you have to limit the current to the value specified in the datasheet to keep from destroying it. So if you have an LED with a 1.7V drop and a current rating of 30mA, you find your current limiting resistor by the following method:  $(5.0V - 1.7V) / .030A = 110\Omega$  resistor.

In the case of our I2C pins, the rating listed in the datasheet is the  $V_{OL}$  and the  $I_{OL}$ . This is from the Atmel AT30TS750 Temperature Sensor datasheet that we'll be using in our first I2C component module coming up.

Symbol	Parameter	Condition	Value
$V_{OL}$	Output Low Voltage	$I_{OL} = 3mA$	0.4V

So, in this case the calculation is  $(5.0V - 0.4V) / .003A = 1533\Omega$ . That represents the lowest possible pullup resistor value, commonly designated  $R_P$  you can use, because anything less would burn out your I2C pins. The value of the resistor would be larger with a smaller  $I_{OL}$ , so the smallest  $I_{OL}$  on the bus would determine the minimum  $R_P$ .

If you were using a 3.3V supply, and your I2C device had a  $V_{OL}$  of 0.4V and an  $I_{OL}$  of 2.1mA, what would your minimum resistor value be?

Hover mouse to read answer:  $(3.3V - 0.4V) / 0.0021A = 1380\Omega$

### I2C Bus Capacitance



There is a formula, derived from the RC time constant, that brings all of this together (see section 7.1 of the I2C Manual ([http://www.nxp.com/documents/user\\_manual/UM10204.pdf](http://www.nxp.com/documents/user_manual/UM10204.pdf)) for the algebra involved). It looks like this...

$$R_{P(max)} = \frac{t_r}{0.8473 \cdot C_{BUS}}$$

The value of  $t_r$  is the maximum allowable rise time of the I2C signal. If you think about it without all the numbers... the larger the resistor, the longer it takes for the capacitor that is your circuit to charge, the longer it takes from the signal to rise to a logic high. The faster you need to rise, meaning the speed at which you're running your I2C circuit, the smaller the  $t_r$  becomes. The value of  $t_r$  for the common I2C modes are as follows...

I2C Mode Name	I2C Speed	Rise Time Value $t_r$
Standard Mode	100kHz	1000nS
Fast Mode	400kHz	300nS
Ultra Fast Mode	1000kHz	120nS


We have all the parts we need to determine our maximum  $R_p$ . Let's choose the 400kHz Fast Mode and use the values we found for the Education Shield. Remember that all our values displayed so far have been listed in nice big "nanoseconds" and "picofarads" so we have to adjust the nanoseconds to seconds ( $\times 10^{-9}$ ) and picofarads to farads ( $\times 10^{-12}$ ).

$$SCLR_{P(max)} = \frac{300nS \times 10^{-9}}{0.8473 \cdot 17.25pF \times 10^{-12}} = 20525.56\Omega$$

$$SDAR_{P(max)} = \frac{300nS \times 10^{-9}}{0.8473 \cdot 19.14pF \times 10^{-12}} = 18498.74\Omega$$

An 18K resistor represents the largest resistor we could use for pullup resistors on the I2C and SPI Education Shield (because 18K would work for both buses, no need to use two different values). Conversely, a 1K5 resistor is the smallest value we could use without burning up the I2C pins of our devices. We want to hit a value somewhere in the middle, and that is why when you look at the schematic excerpt of the I2C subsystem from the Education Shield at the very top of page, the pull up resistors are 10K.

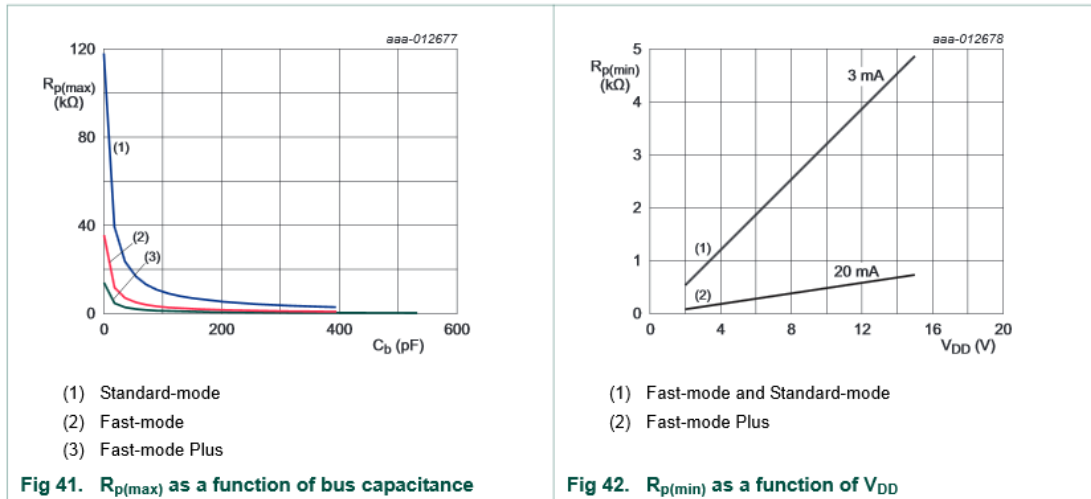These two aspects of pull up resistor specification are captured in these two charts from the NXP I2C Manual (note: the Arduino is not capable of Fast-mode Plus)...



PULL UP RESISTOR SPECIFICATIONS

### $C_{BUS}$ Greater Than 200pF

In the event that you have a bus capacitance that exceeds 200pF **and** you are attempting to drive the I2C bus at Fast Mode speed or greater, pull up resistors will no longer be sufficient, and you'll need to investigate the use of a current source or switched resistor circuit to supply the SDA and SCL logic high voltage necessary to achieve those signalling speeds with that much  $C_{BUS}$ .

### I2C Pull Up Resistor Bottom Line

If you're working with a single chip on a breadboard, just use whatever resistor value you have on hand from 4K7 to 10K for your SDA and SCL signals and you'll be fine. Going through all the calculations above only becomes critical when you begin laying out your own PCBs and start loading more than one or two I2C devices into your circuit. You can see that the difference of 1.89pF between the SCL and the SDA buses above lowered the allowable resistance by over 2000Ω. Consequently, long PCB traces (or even worse using a ribbon cable to attach a device to the bus) or adding multiple devices with their pin capacitance will have a very significant effect on your R<sub>p</sub> value.



Share this:

- (<https://rheingoldheavy.com/i2c-pull-resistors/?share=facebook&nb=1>)
- (<https://rheingoldheavy.com/i2c-pull-resistors/?share=reddit&nb=1>)
- (<https://rheingoldheavy.com/i2c-pull-resistors/?share=twitter&nb=1>)
- (<https://rheingoldheavy.com/i2c-pull-resistors/?share=google-plus-1&nb=1>)

Dan (<https://rheingoldheavy.com/author/grunthos/>) January 16, 2015

05. I2C Basics (<https://rheingoldheavy.com/category/education/i2c-basics/>), Education (<https://rheingoldheavy.com/category/education/>), Education Shield Tutorials (<https://rheingoldheavy.com/category/education/education-shield-tutorials/>), P.I2C General (<https://rheingoldheavy.com/category/product-categories/p-i2c-general/>)

11501 0

### One thought on "I2C Pull Up Resistors"

Pingback: Our First Call In Show | The Amp Hour Electronics Podcast (<http://www.theamphour.com/274-our-first-call-in-show/>)

Comments are closed.

[I2C BASICS \(HTTPS://RHEINGOLDHEAVY.COM/I2C-BASICS/\)](https://rheingoldheavy.com/i2c-basics/)

[I2C SIGNALS](https://rheingoldheavy.com/i2c-signals/) (HTTPS://RHEINGOLDHEAVY.COM/I2C-SIGNALS/)



(<https://twitter.com/rheingoldheavy>)

All content is generated and owned by me. © Dan Hienzsch



